

ELEC5280 Final Project Presentation

**XU Jiashuai, LIU Yichen
03/06/2024**

Outline

- **Architecture of the Receiver**
- **Workload Distribution**
- **Design of Building Blocks**
 - i. LNA
 - ii. Mixer
 - iii. IF Amplifier
 - iv. Receiver System
- **Conclusion**

Outline

- **Architecture of the Receiver**


- **Workload Distribution**

- **Design of Building Blocks**

- i. LNA
- ii. Mixer
- iii. IF Amplifier
- iv. Receiver System

- **Conclusion**

Architecture of the Receiver

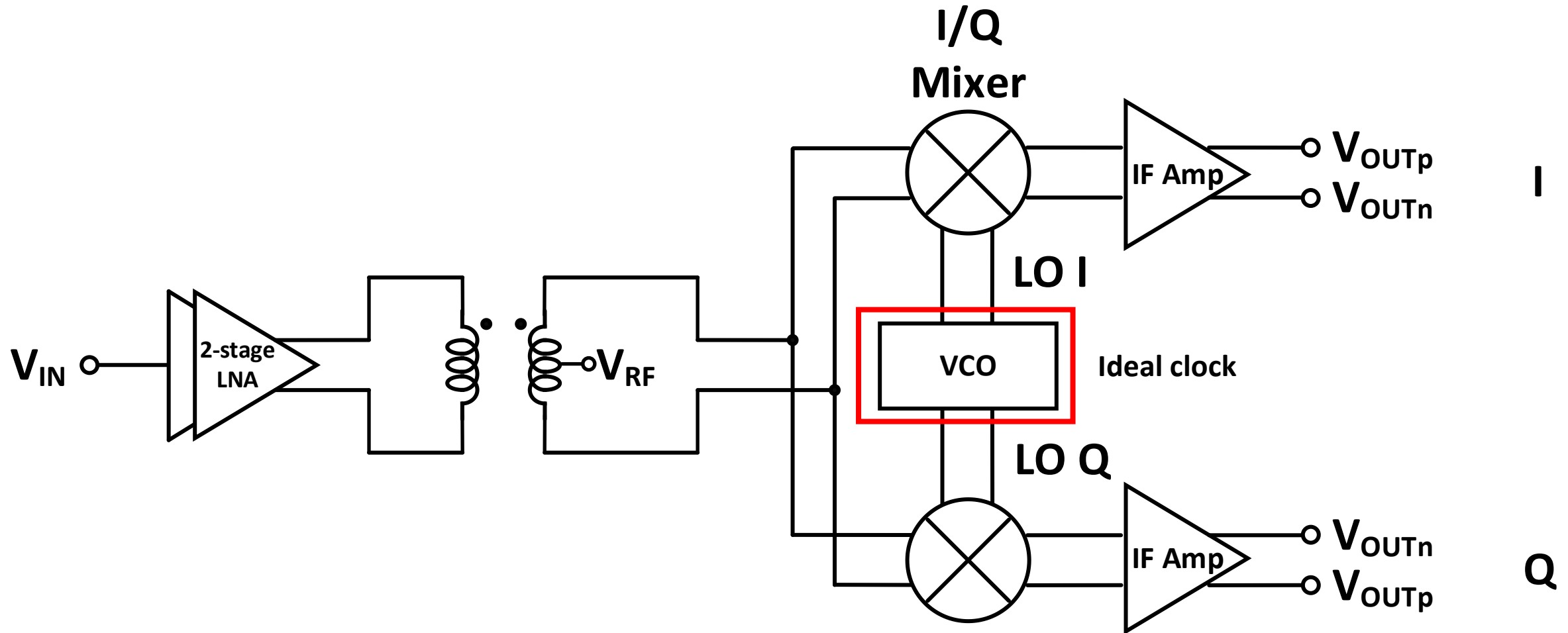

Outline

➤ **Architecture of the Receiver**

➤ **Workload Distribution**

➤ **Design of Building Blocks**

- i. LNA
- ii. Mixer
- iii. IF Amplifier
- iv. Receiver System

➤ **Conclusion**

Workload Distribution (Specifications)

Task	LNA	Mixer	IF Amplifier	Report + System Simulation	Specifications
Person in charge	Yichen	Jiashuai	TA	ALL	/
Noise Figure (dB)	2.9 (<5)	9.8 (<20)	5.1 (<10)	4.0	< 7
Gain (dB)	12.9 (>9)	-1.9 (>-5)	14.6 (>20)	26.7	> 25
IIP3 (dBm)	-5 (>-20)	2.5 (>0)	-5.1 (>-10)	-17.4	> -20
Power Consumption (mW)	19.7 (<20)	6.75 (<15)	1.76 (<10)	28.2	< 30
S11 (dB)	/	/	/	-22.5	< -12
EVM	/	/	/	on-going	< 15%

Outline

➤ **Architecture of the Receiver**

➤ **Workload Distribution**

➤ **Design of Building Blocks**

i. LNA


ii. Mixer

iii. IF Amplifier

iv. Receiver System

➤ **Conclusion**



i. LNA: schematic

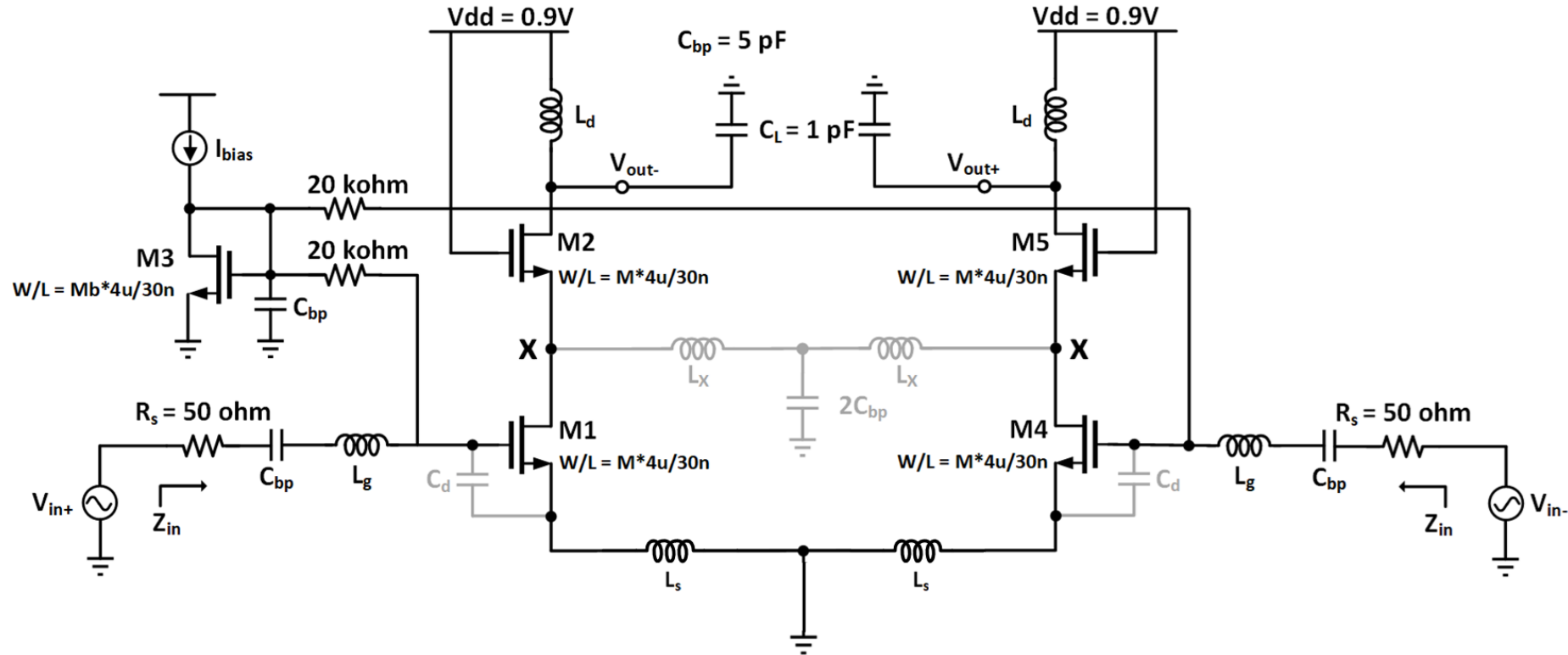

- One standard differential low noise amplifier with inductive load
- Impedance matching: L_s and L_g
- C_d : decoupling Q from C_{gs} → gate induced current noise ↓
- L_x : reduce the influence of parasitic C_x → noise of M2 relatively decrease ↓

$$Z_{in} = \frac{g_m L_s}{C_{gs}} + s \left(L_s + L_g + \frac{1}{C_{gs}} \right)$$

i. LNA: design considerations

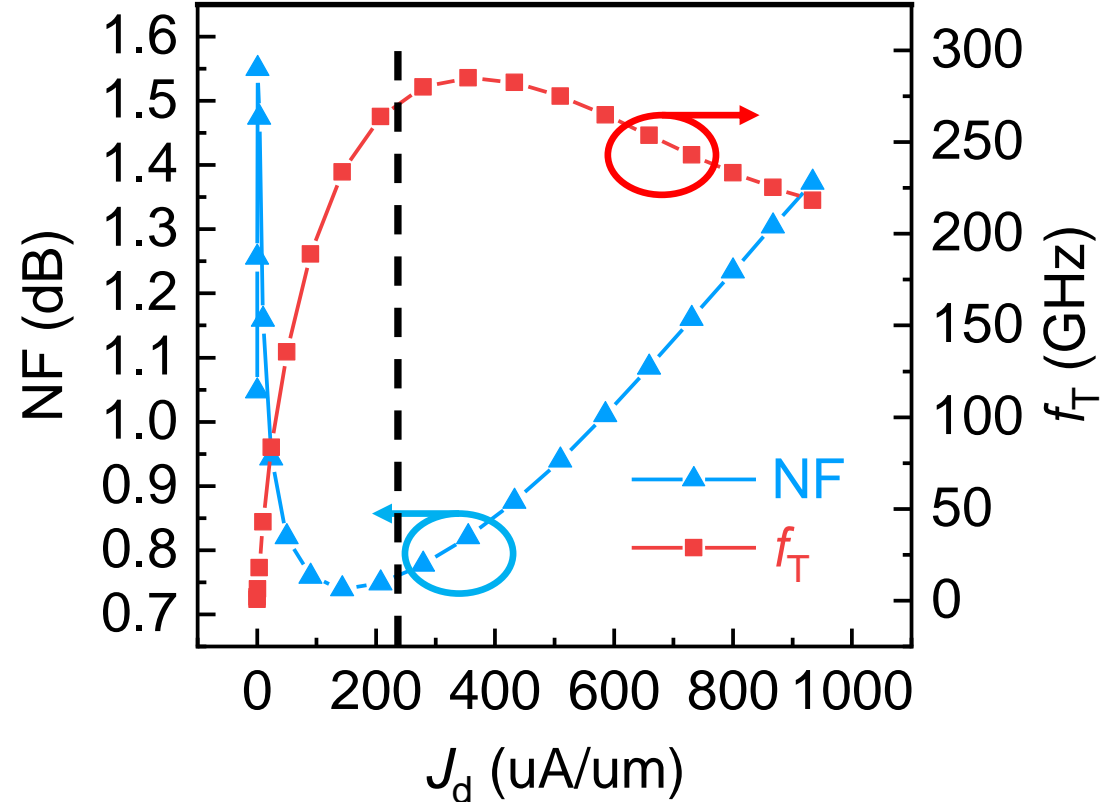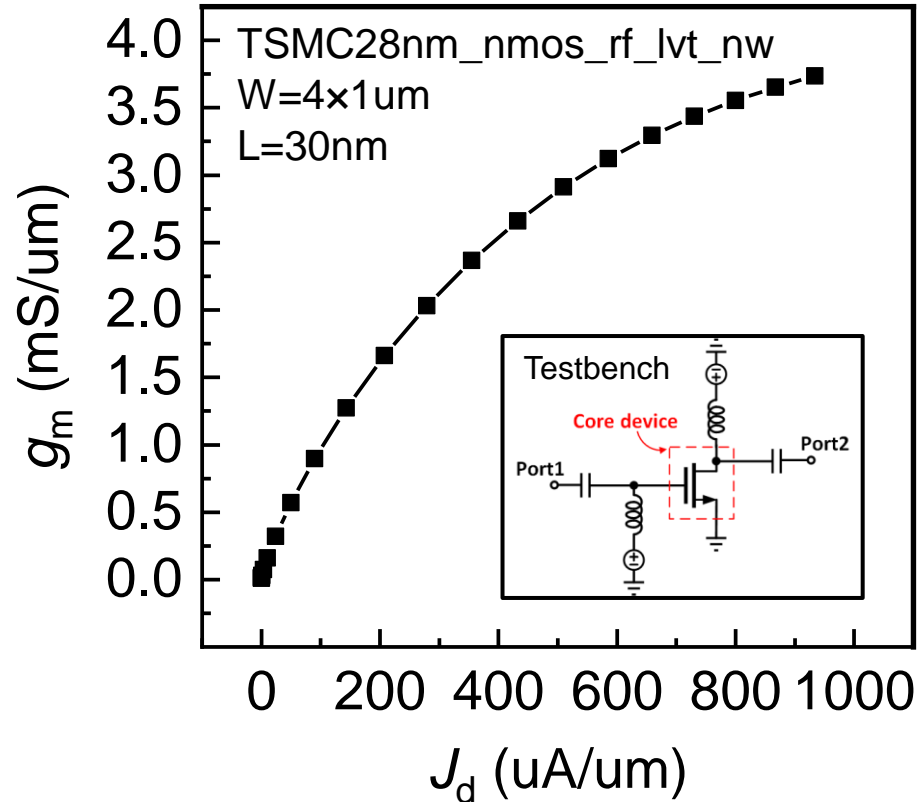


- DC operating point selection: trade-off between Gain and NF
- Gain: larger with larger g_m
- NF: trade off between thermal noise and drain current noise
- Better linearity when g_m saturates

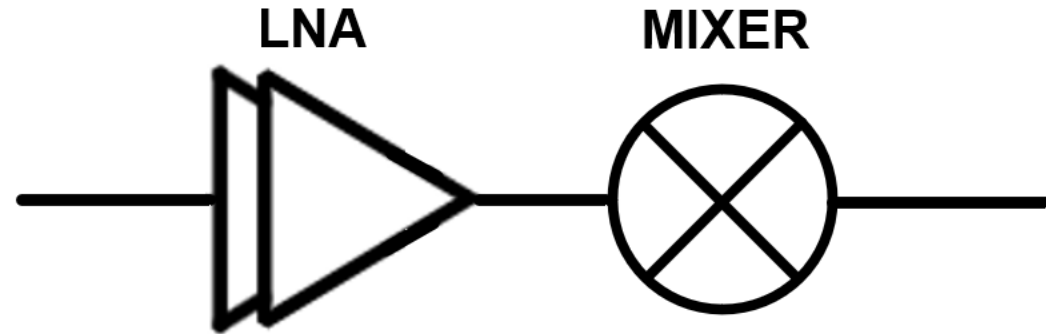i. LNA: design considerations


$$NF_{tot} = NF_{LNA} + \frac{NF_{MIXER} - 1}{A_{P_{LNA}}}$$

$$\frac{1}{IP_{3,tot}^2} = \frac{1}{IP_{3,LNA}^2} + \frac{\alpha_{LNA}^2}{IP_{3,MIXER}^2}$$







- System Gain: sum of all blocks
- System NF: mainly determined by LNA
- System IIP3: mainly determined by MIXER due to nearly 13dB gain of LNA

i. LNA: simulation results

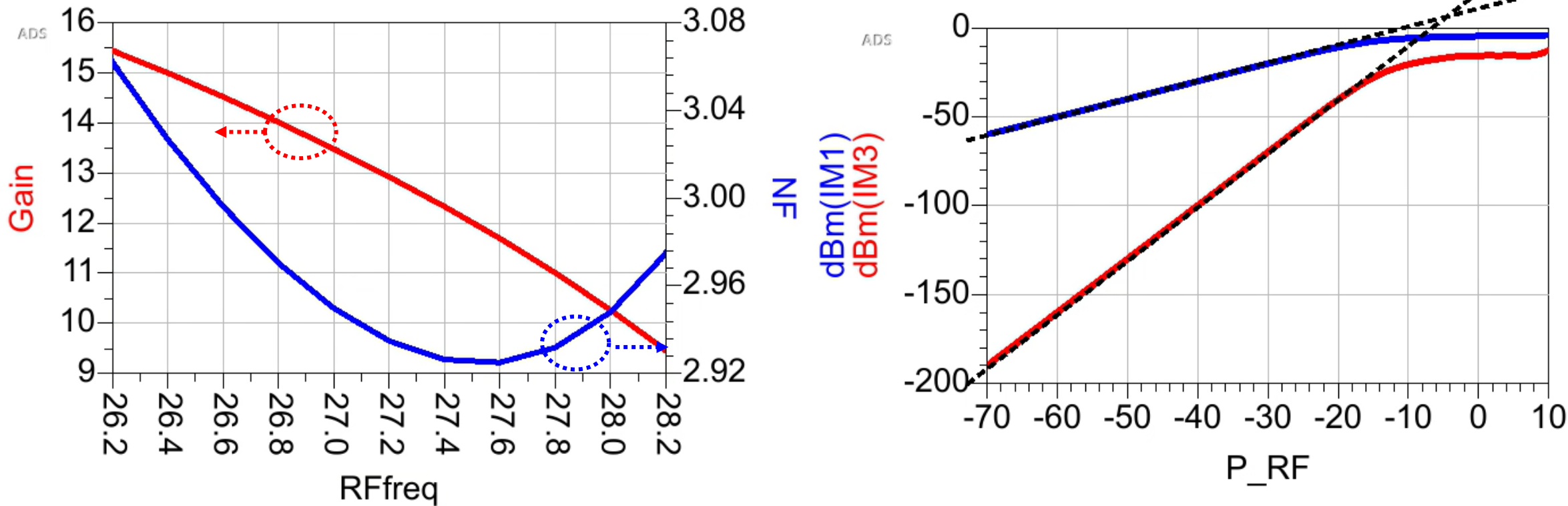

Part	Noise Figure (dB)	Gain (dB)	IIP3 (dBm)	Power Consumption (mW)
LNA	2.9(<5)	12.9 (>9)	-5.0 (>-20)	19.7 (<20)


ii. Mixer: schematic

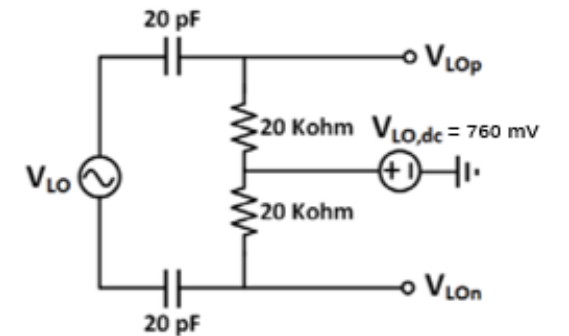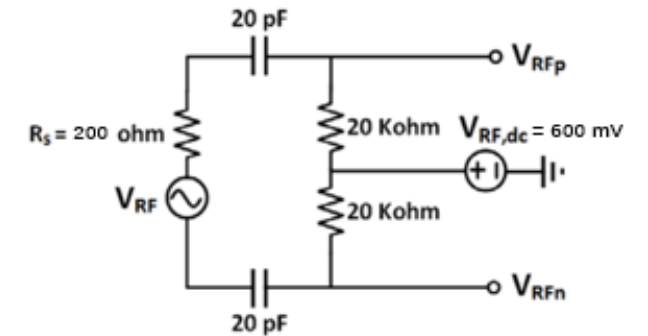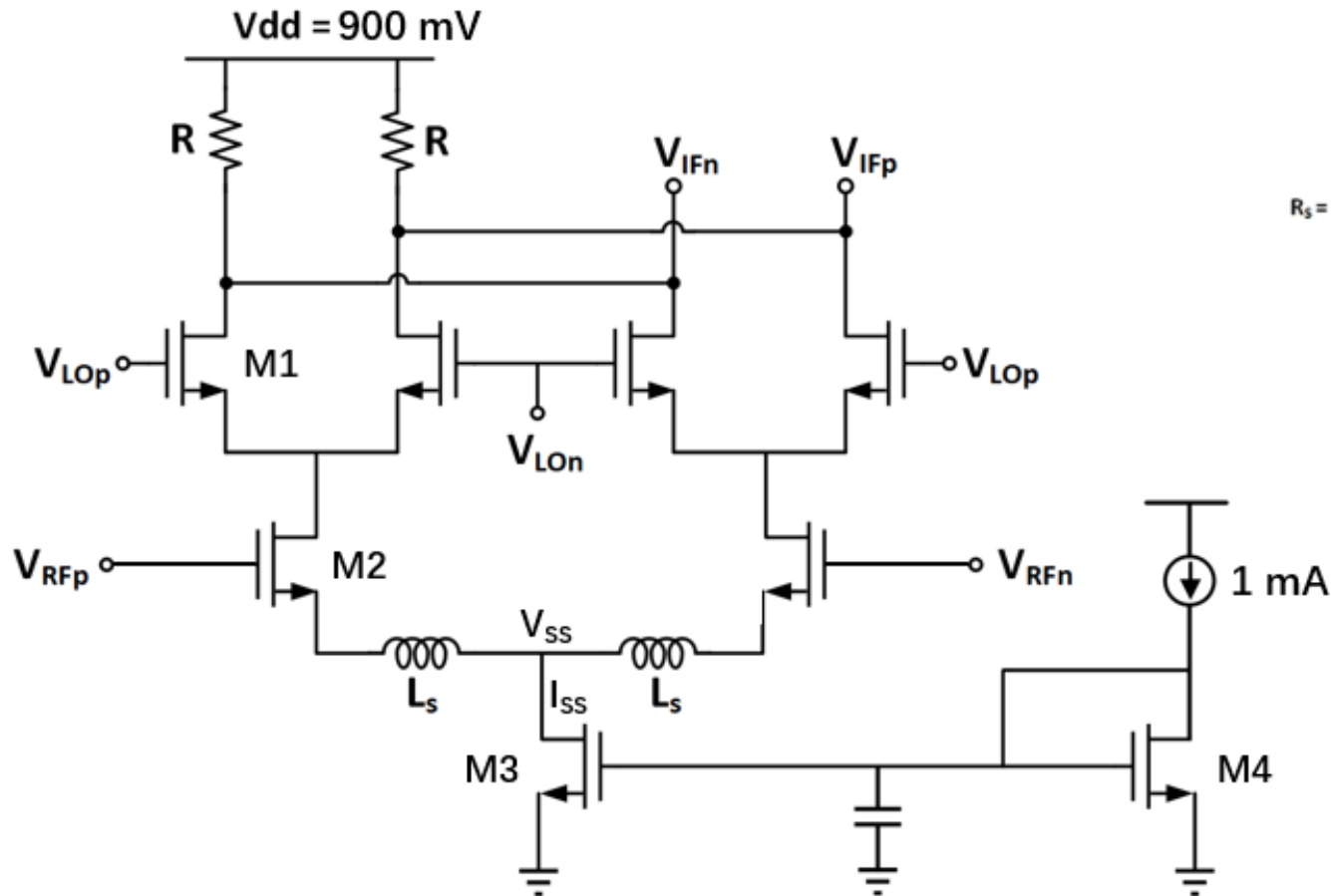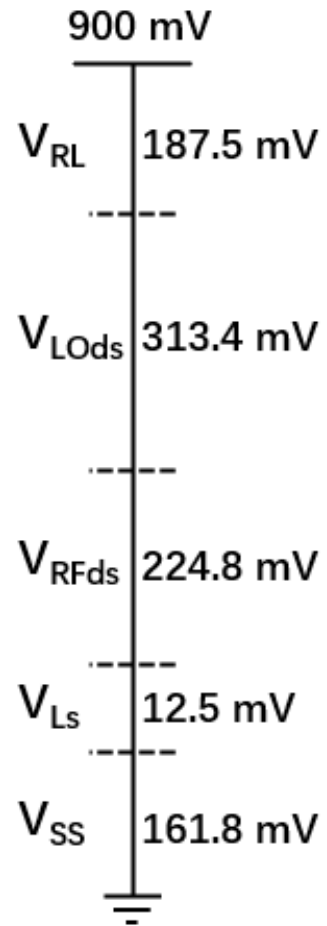

$$Gain = \frac{2}{\pi} g_{mRF} R_L$$

$$IIP3 = 4 \sqrt{\frac{2}{3} \frac{I_{dsRF}}{\mu_n C_{ox}}}$$



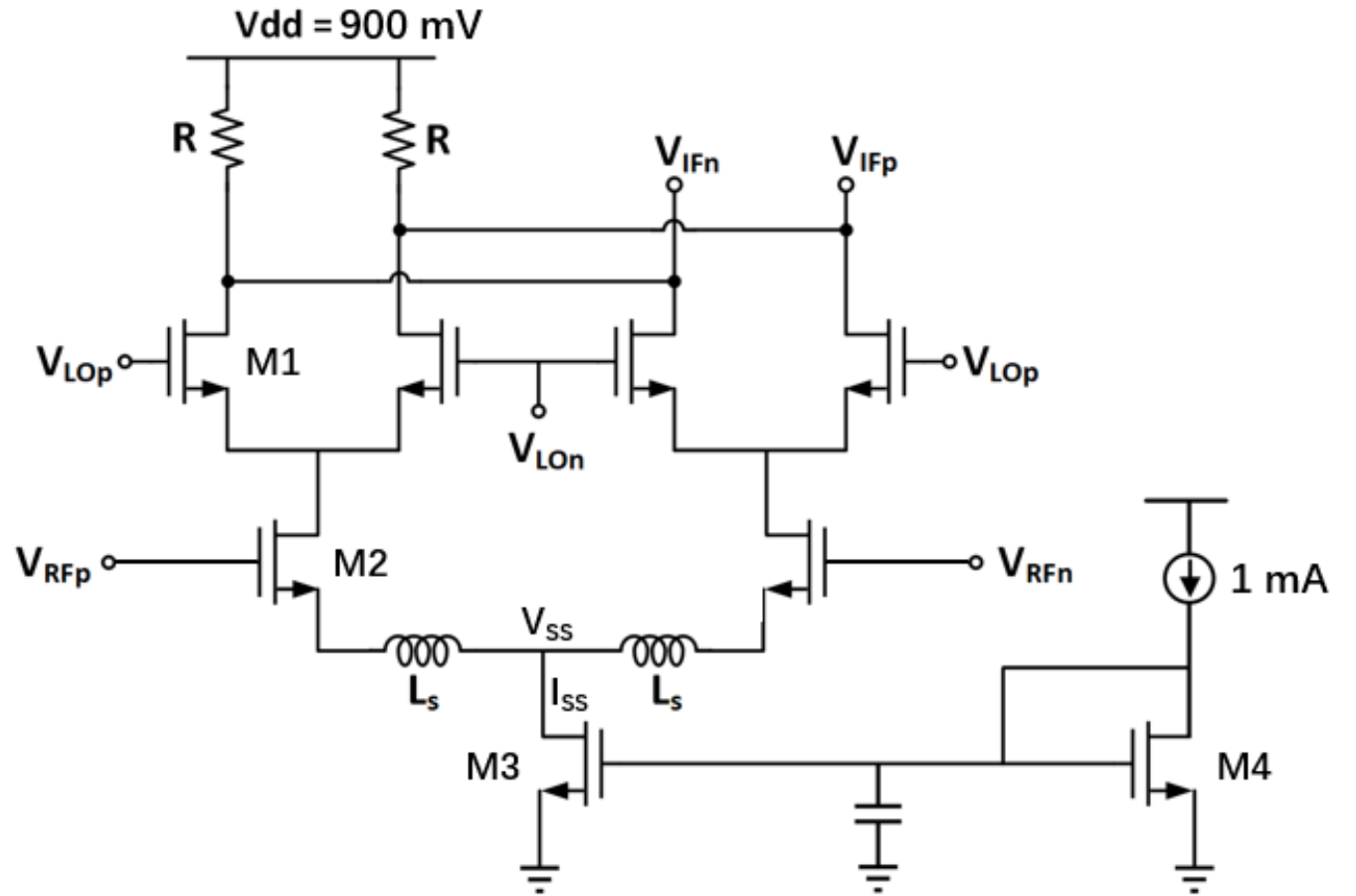
$$P3 = 4 \sqrt{\frac{2}{3} (V_{gs} - V_{TH})}$$



$$NF = 10 \log \left(2 + \frac{4\gamma}{g_m R_s} + \frac{\pi^2}{2g_m^2 R R_s} \right)$$

Mixer power: 8mW (<4mW per one)

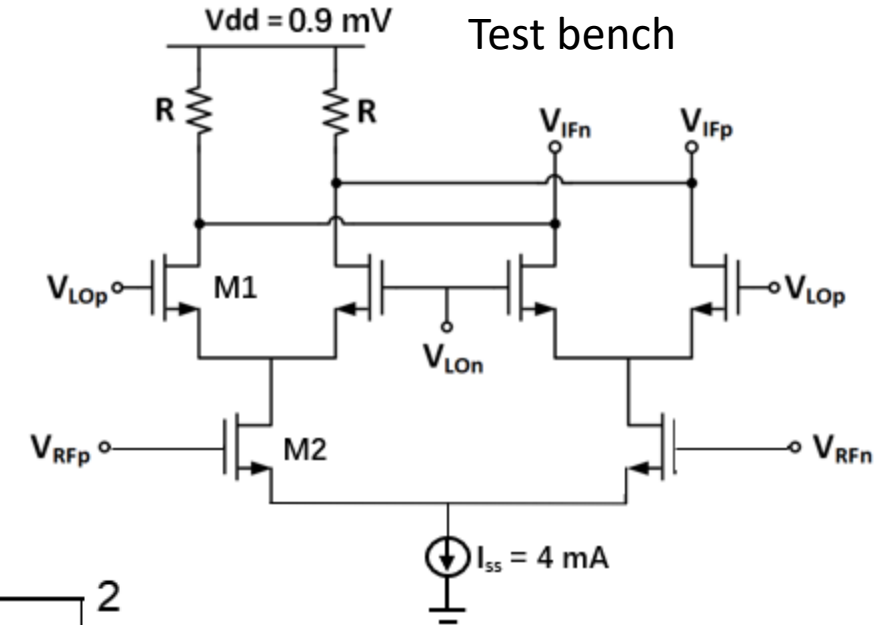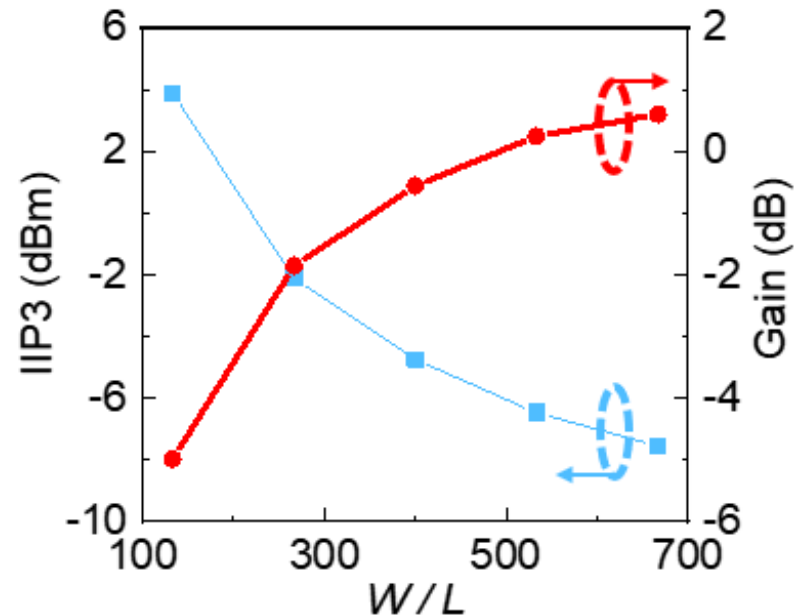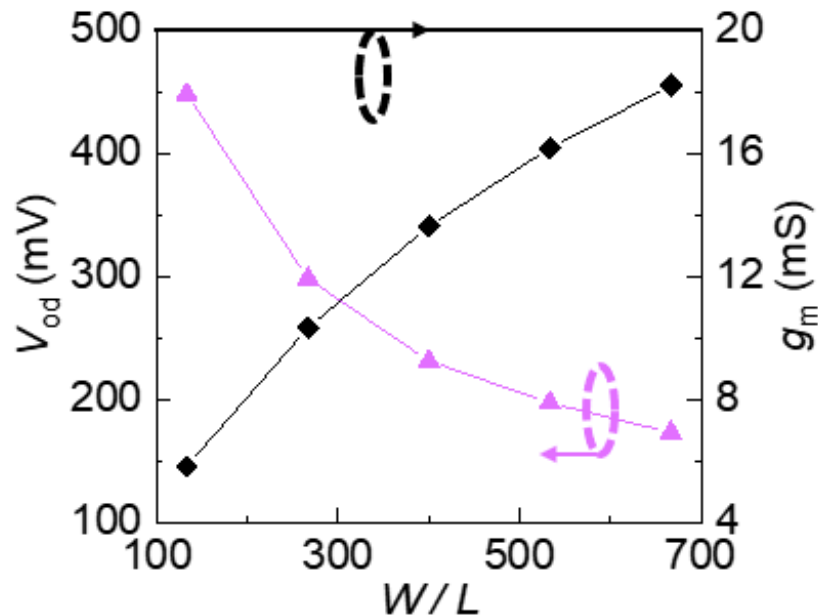
$$\text{Power} = V_{DD}I_{SS} \quad I_{SS} < 4.4\text{mA}$$






- W/L of M2 is chosen around 500 with fixed $I_{SS} = 4 \text{ mA}$.
- Gain $\sim 0 \text{ dB}$
- IIP3 $\sim -6 \text{ dBm}$
- $g_m \sim 16 \text{ mS}$
- $V_{od} \sim 200 \text{ mV}$

ii. Mixer: design process

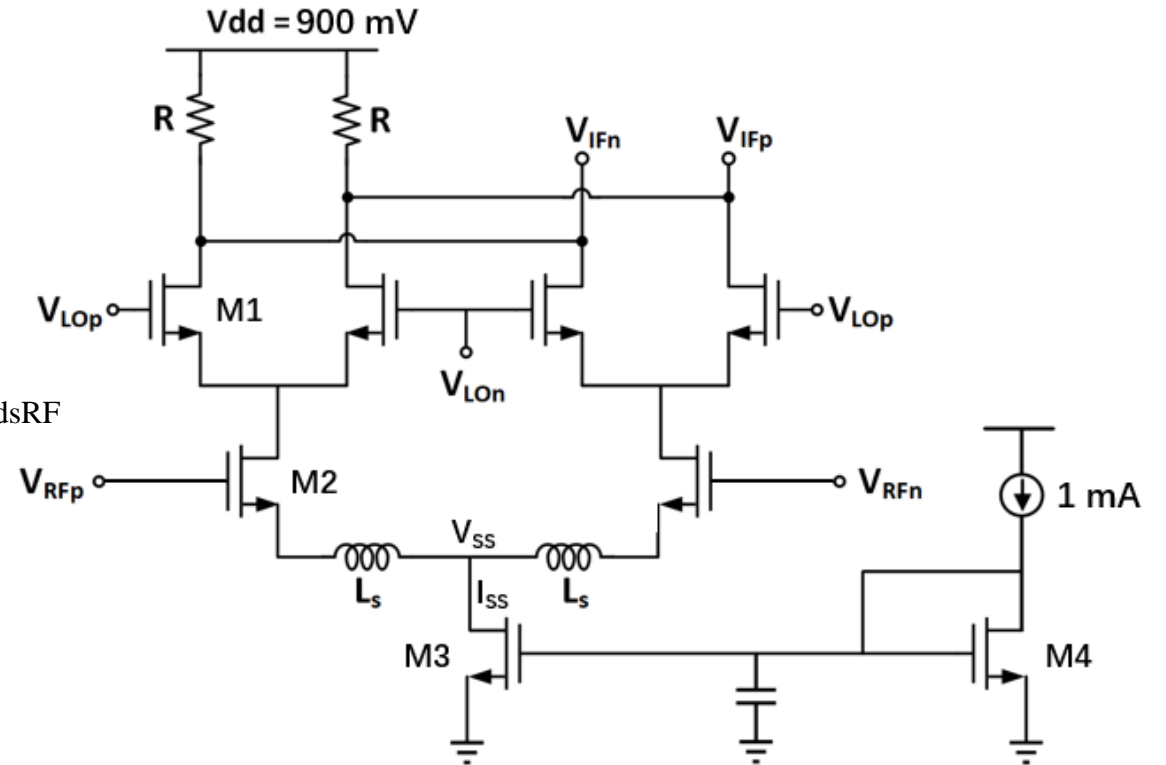1. Set $I_{SS} = 4\text{mA} \rightarrow \text{power} < 4\text{mW}$
2. Select suitable $\frac{W}{L'}$ for M3 with suitable $g_m \rightarrow \text{headroom}$
3. Set $R_L = 100\Omega \rightarrow \text{headroom}$
4. Select initial $\frac{W}{L'}$ for M2 with suitable $g_{mRF} \rightarrow \text{IIP3, gain, and } V_{dsRF}$
5. Select initial $\frac{W}{L'}$ for M1 with suitable $g_{mLO} \rightarrow V_{dsLO}$
6. Optimize L_s until IIP3 and gain are big.




ii. Mixer: simulation results

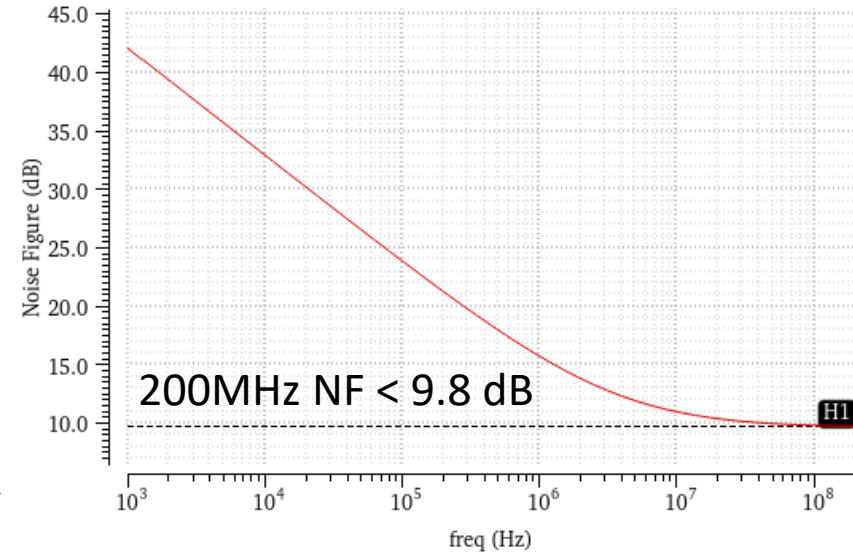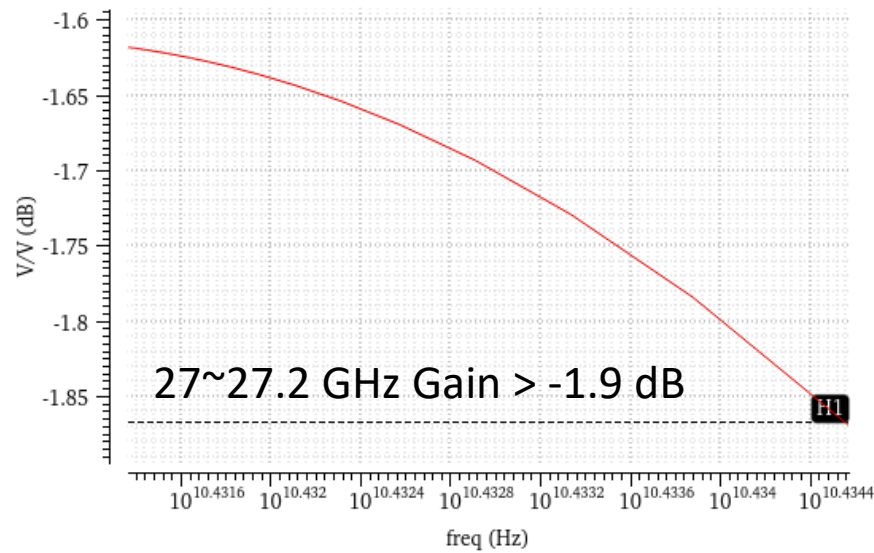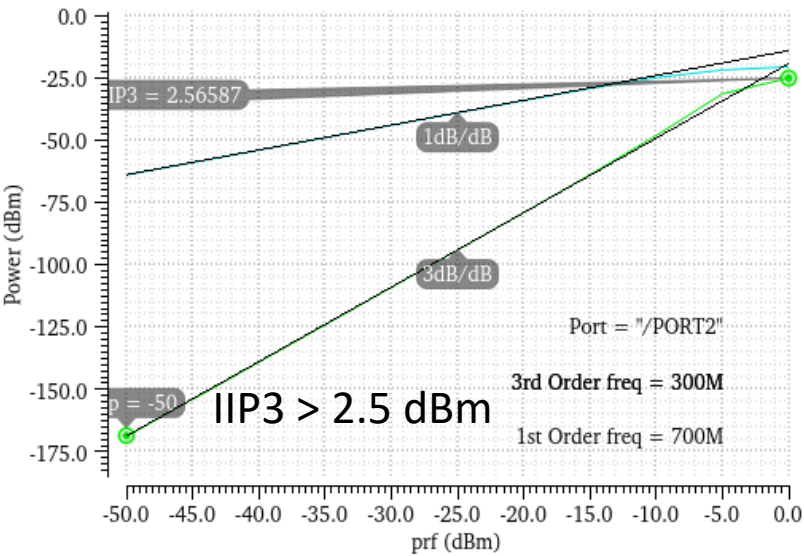


Part	Noise Figure (dB)	Gain (dB)	IIP3 (dBm)	Power Consumption (mW)
Mixer	9.8 (<10)	-1.9 (>-5)	2.5 (>0)	6.75

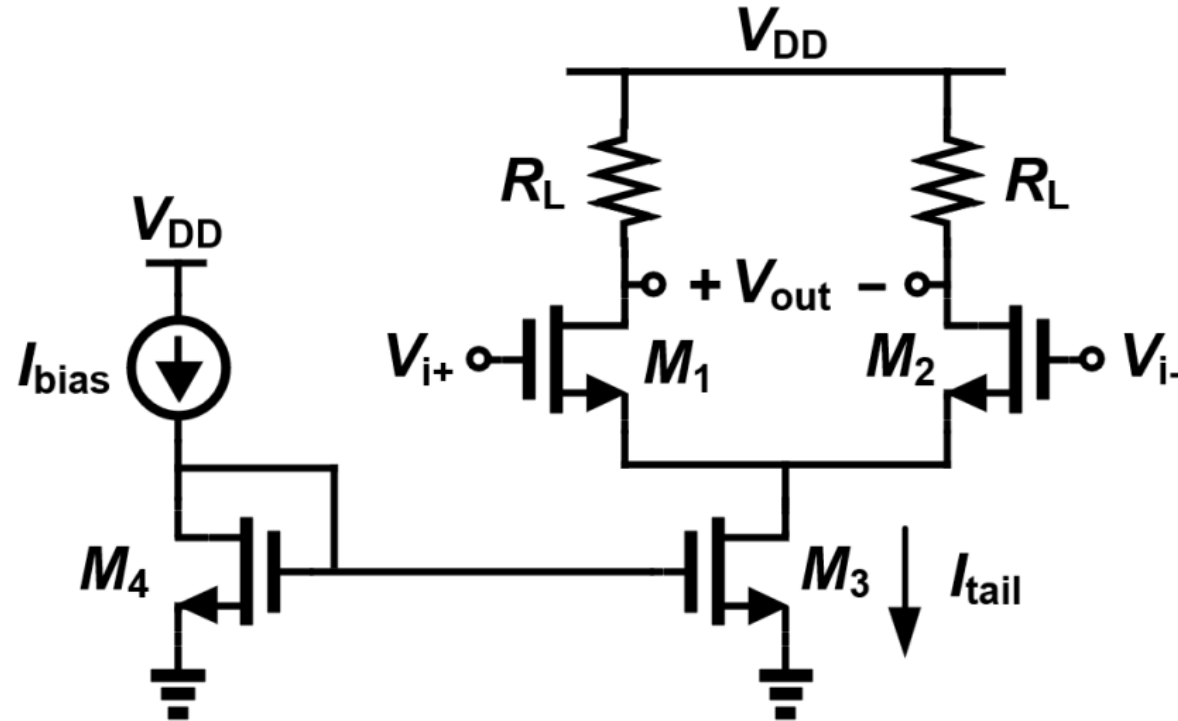iii. IF Amplifier (given by TA) : schematic




- Simple resistor load differential structure
- Focus on large gain design to amplify the BB signal

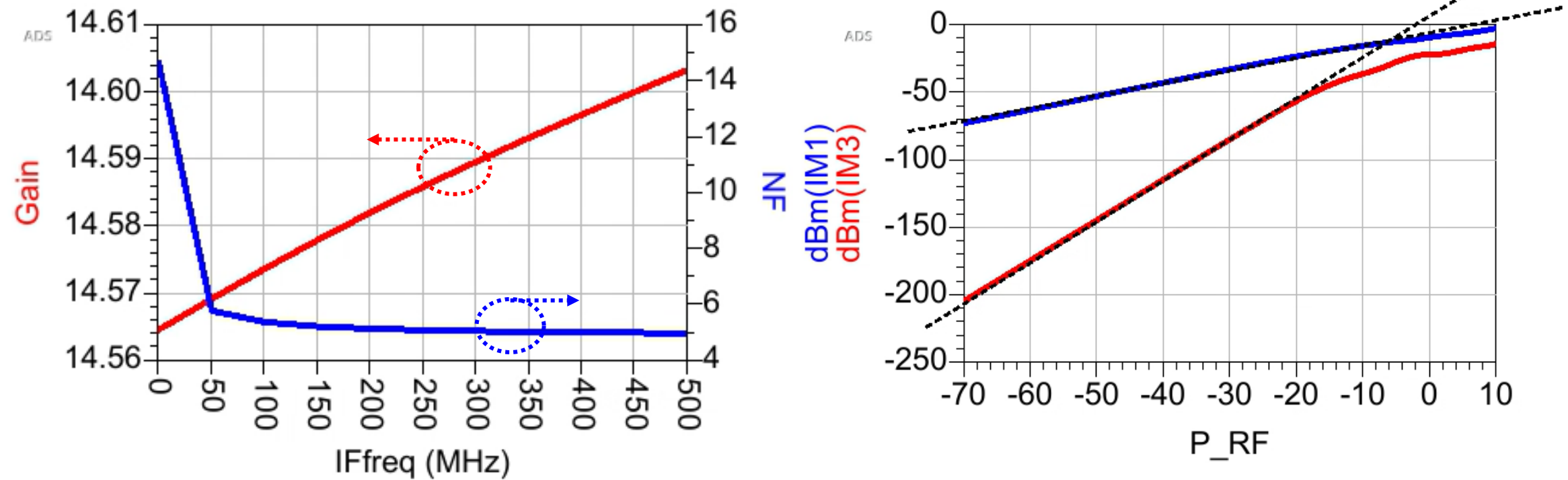iii. IF Amplifier (given by TA) : simulation results




Part	Noise Figure (dB)	Gain (dB)	IIP3 (dBm)	Power Consumption (mW)
IF_Amplifier	5.1 (<10)	14.6 (>20)	-5.1 (>-10)	1.76 (<10)



iv. Receiver system

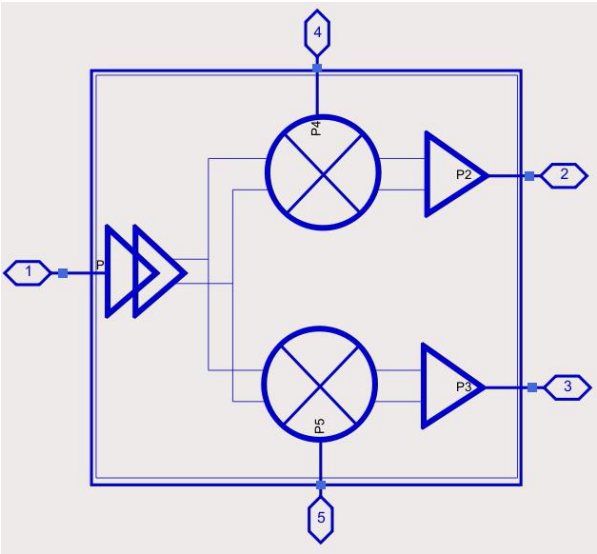

ADS Symbol



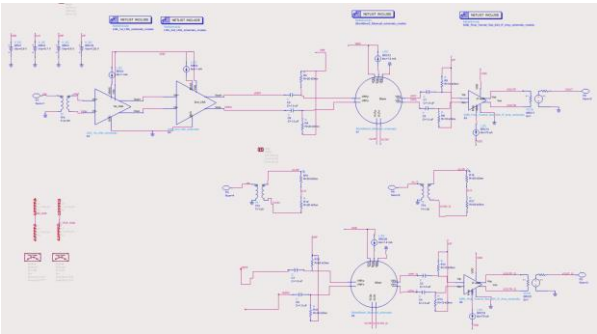


ADS circuit

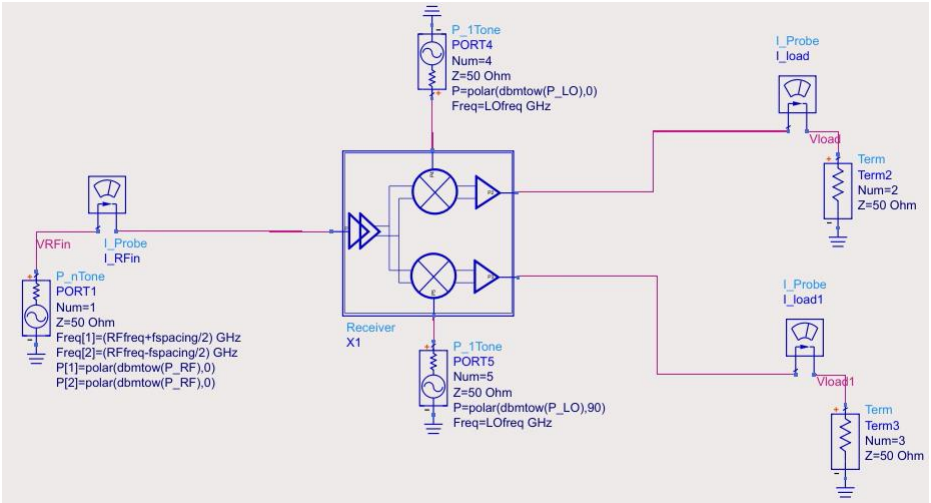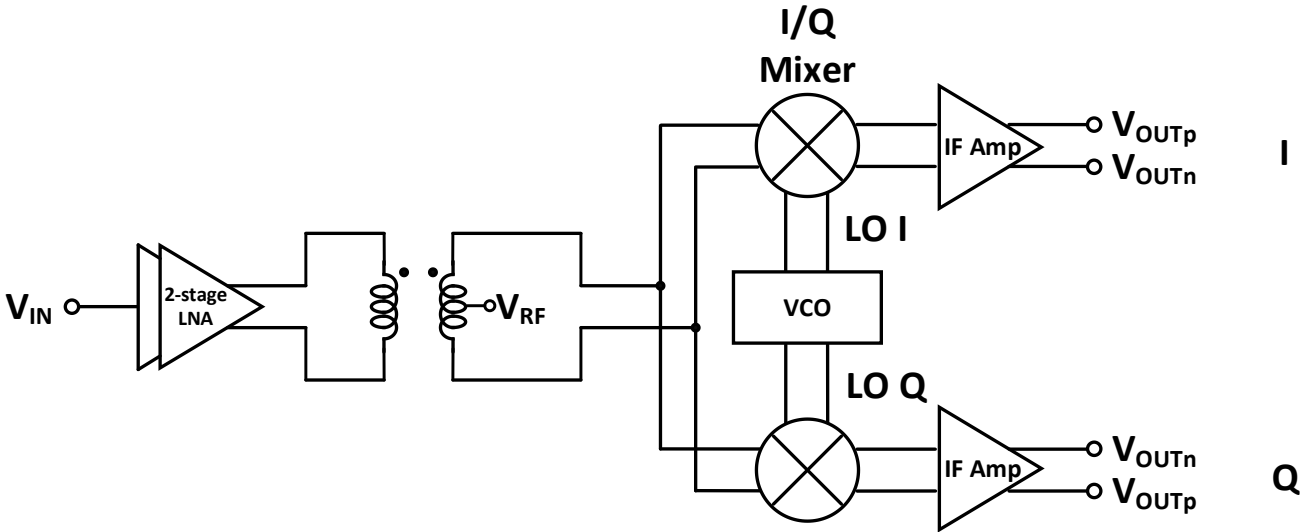


ADS test bench

iv. Receiver system: simulation results

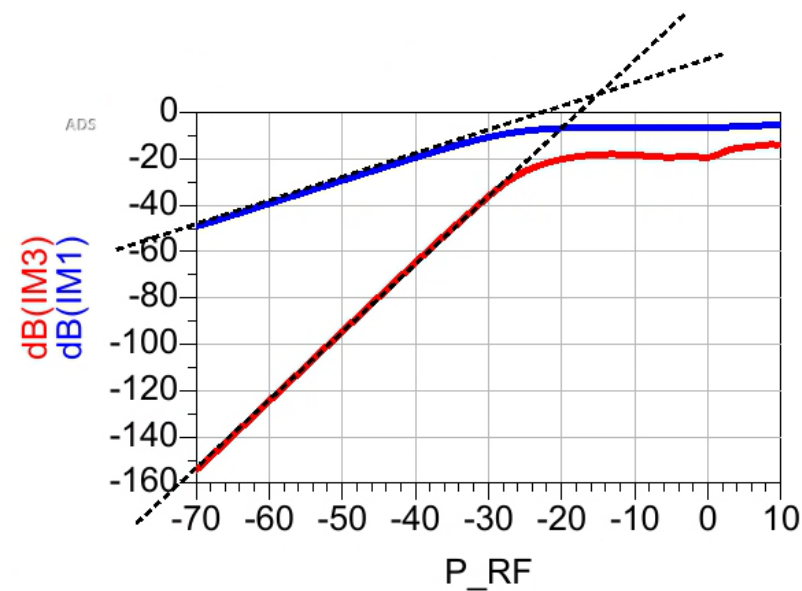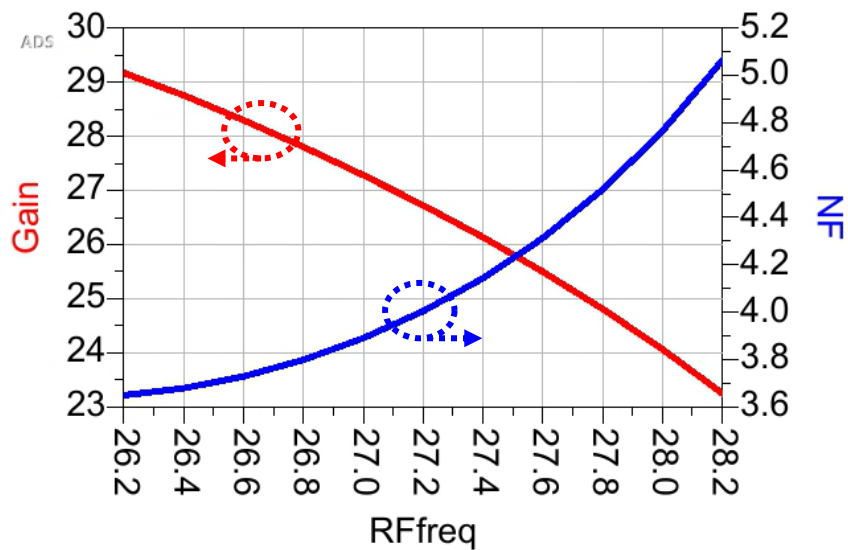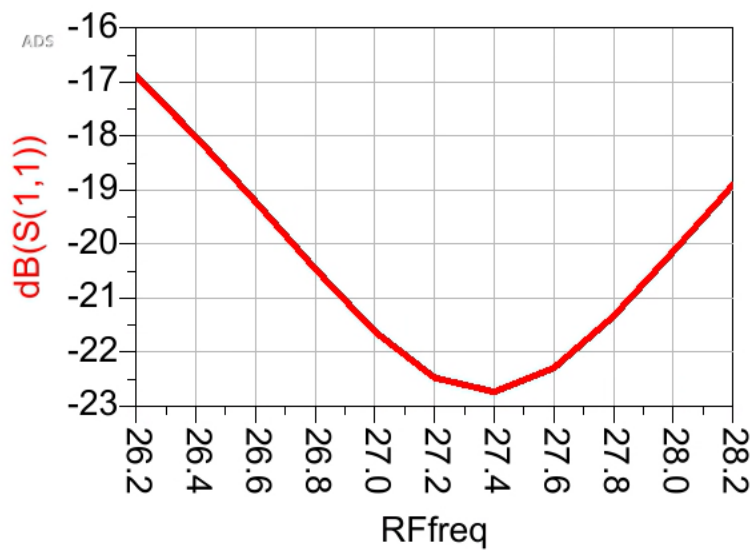

Part	S11(dB)	Noise Figure (dB)	Gain (dB)	IIP3 (dBm)	Power Consumption (mW)
Receiver	-22.5 (<-12)	4.0 (<10)	26.7 (>25)	-17.4 (>-20)	28.2 (<30)

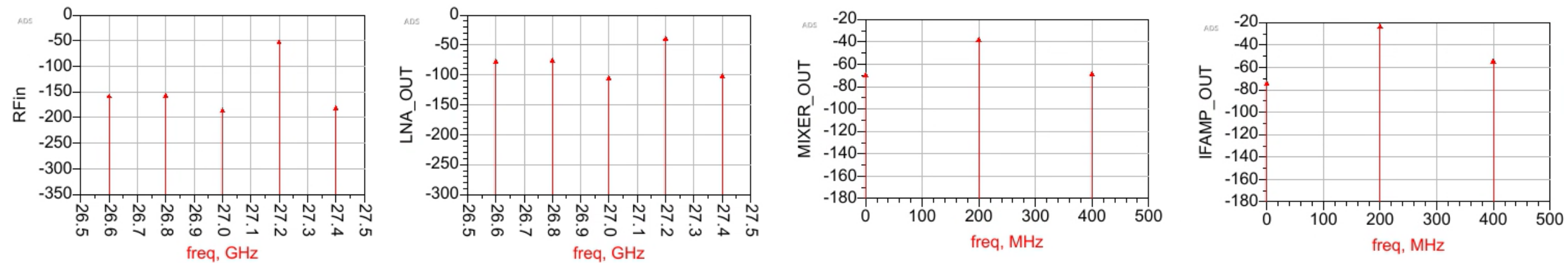iv. Receiver system: simulation results - Spectrum



Part	S11(dB)	Noise Figure (dB)	Gain (dB)	IIP3 (dBm)	Power Consumption (mW)
Receiver	-22.5 (<-12)	4.0 (<10)	26.7 (>25)	-17.4 (>-20)	28.2 (<30)

Outline

➤ **Architecture of the Receiver**

➤ **Workload Distribution**

➤ **Schematic of Building Blocks**

- i. LNA
- ii. Mixer
- iii. IF Amplifier

➤ **Simulation Results**

- i. LNA
- ii. Mixer
- iii. IF Amplifier
- iv. Receiver System

➤ **Conclusion**

Conclusion

Parameters	Specifications	Simulations
Noise Figure (dB)	< 7	4.0
Conversion Voltage Gain (dB)	> 25	26.7
S11 (dB)	< -12	-22.5
IIP3 (dBm)	> -20	-17.4
Power Consumption (mW)	< 30	28.2
EVM	< 15%	On-going

Acknowledgement

We would like to thank Sarah, Shawn, and Elise for their help of software operation and debug, and Oscar for useful discussions.